

# Architecture : microprocessor work

**H. Cassé** <[casse@irit.fr](mailto:casse@irit.fr)>


*Some schemes are gracefully provided wikipedia and openclipart  
under open license.*



UNIVERSITÉ  
TOULOUSE III  
PAUL SABATIER




Faculté  
Sciences  
et Ingénierie

 
 
# Introduction

- today, any device
  - automotive, aeronautics, space
  - domestic appliances, traffic lights, ...
  - contains a microprocessor!
- embedded application
  - software → smart device
  - hardware running the software
  - based on transistors + memory technologies



# Embedded microprocessor market



 


Figure 1: Responses to "My current embedded project's main processor is ...".

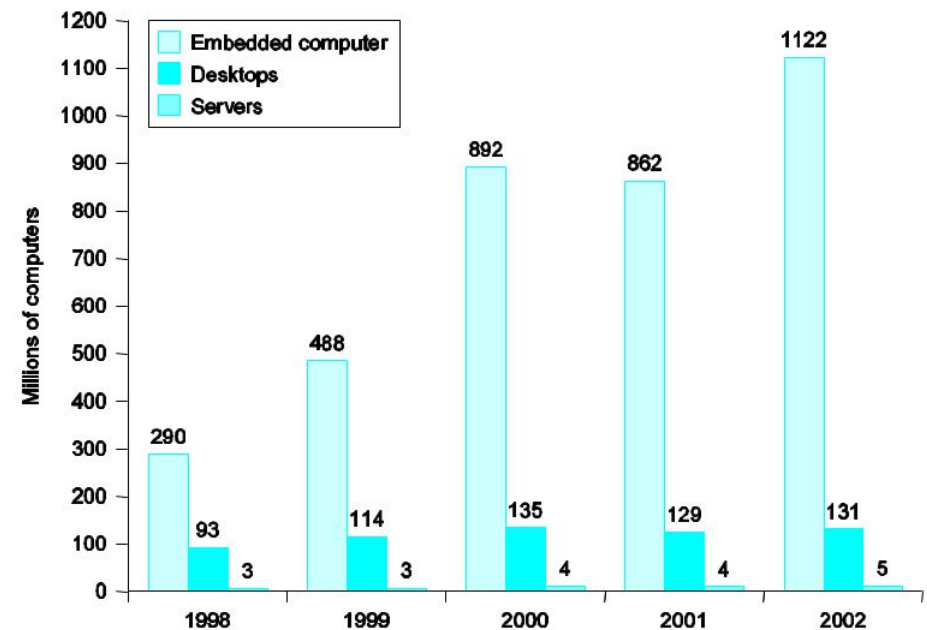


 

 
# Comparison

- Laptop/Desktop
  - 64-bit
  - 1-3 GHz
  - 4-8 GB
  - x86 – Intel, AMD
- Mobile
  - 32/64-bits
  - 1-3 Ghz
  - 0.5-2 Gb
  - ARM – Nvidia, Qualcomm
- Embedded
  - 8, 16, 32, 64-bit
  - 10-500 MHz
  - 1–100 MB
  - AVR, TriCore, ARM, Sparc, Mips, x86 (32-bit), PowerPC, ...
  - DSP, FPGA





# Von Neuman's machine

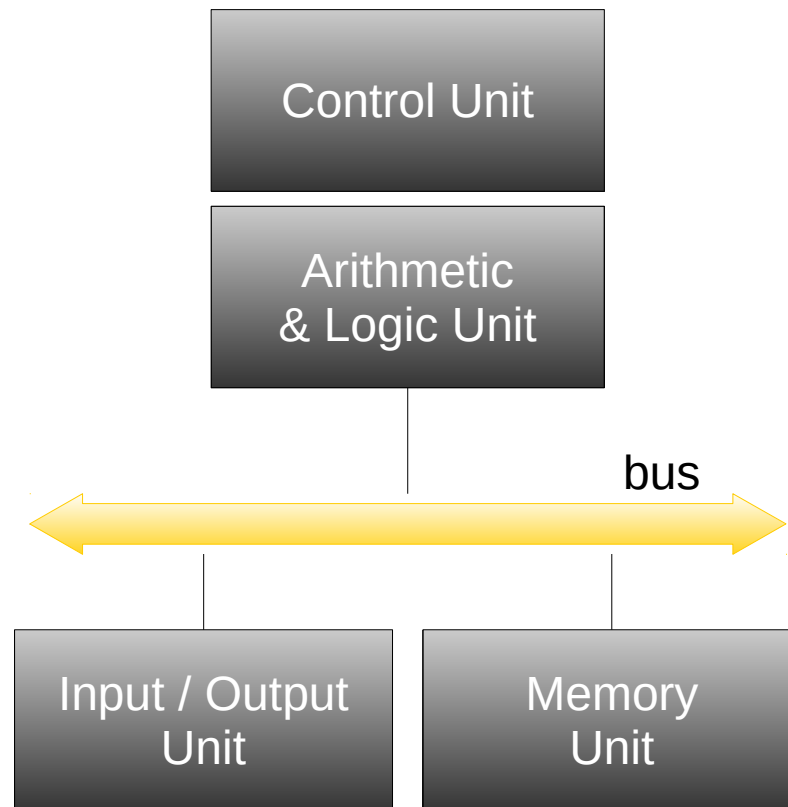


## loop

- (0) read instruction
- (1) read operands
- (2) compute
- (3) write result


 
# Overview

- Introduction
- **Making basic circuits**
- Making the memory
- Making the processor
- Conclusion



# How to implement it?

- number encoding – bit (Binary digit)

- base-2 numbers – 0 or 1

- natural number encoding

$$N = (B_n B_{n-1} \dots B_1 B_0)_2$$

$$= B_n 2^n + B_{n-1} 2^{n-1} + \dots + B_1 2^1 + B_0 2^0$$


- integer encoding – 2's complement

- $(-N)$  s.t.  $N + (-N) = 0$

- $(-N)_2 = (\bar{B}_n \bar{B}_{n-1} \dots \bar{B}_1 \bar{B}_0) \pm 1$

- note

 
- $A + B = \text{OR}$ ,  $A \cdot B = \text{AND}$ ,  $\bar{A} = \text{NOT}$



 
# Designing circuits

- $B = \{0, 1\} \rightarrow$  Boolean algebra
- designing circuit = designing Boolean function(s)
  - identifying boolean input
  - writing a truth table
  - express the output in con(dis)junctive normal form
- (B, NOT, AND, OR) complete group
  - any function can be computed as a combination of these operators
- minimization
  - Karnaugh table ( $\leq 6$  inputs)
  - Quine – Mc Cluskey algorithm





# Example: Adder 1-bit

 

$$2 \times C_{\text{out}} + S = A + B + C_{\text{in}}$$

| A | B | C <sub>in</sub> | C <sub>out</sub> | S |
|---|---|-----------------|------------------|---|
| 0 | 0 | 0               | 0                | 0 |
| 0 | 0 | 1               | 0                | 1 |
| 0 | 1 | 0               | 0                | 1 |
| 0 | 1 | 1               | 1                | 0 |
| 1 | 0 | 0               | 0                | 1 |
| 1 | 0 | 1               | 1                | 0 |
| 1 | 1 | 0               | 1                | 0 |
| 1 | 1 | 1               | 1                | 1 |

$$F_{\text{cout}}(A, B, C_{\text{in}}) = \overline{A}BC + A\overline{B}C + ABC\overline{C} + ABC$$


$$F_S(A, B, C_{\text{in}}) = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$$

## Electronic notation

$\overline{A}$  = NOT A




$A \cdot B$  = A AND B

$A + B$  = A OR B

 

   
# How to implement Boolean operator as NOT?

**Convention:** 0 = 0V, 1 = 1.8V or 3.3 or 5V)




MOSFET (Metal-Oxid-Semiconductor Field-Effect Transistor) n-channel

 gate = 0 ==> no current (off)  
gate = 1 ==> current flows  
from source to drain (on)


 
# How to implement Boolean operator as NOT?



## NOT implementation

$V_{dd} = 1$

$V_{ss} = 0$

when  $A = 1$

$T_1$  off

$T_2$  on

$Q = 0$


when  $A = 0$

$T_1$  on


$T_2$  off

$Q = 1$

 CMOS (Complementary Metal–Oxide–Semiconductor)



# Implementing NAND (NOR)

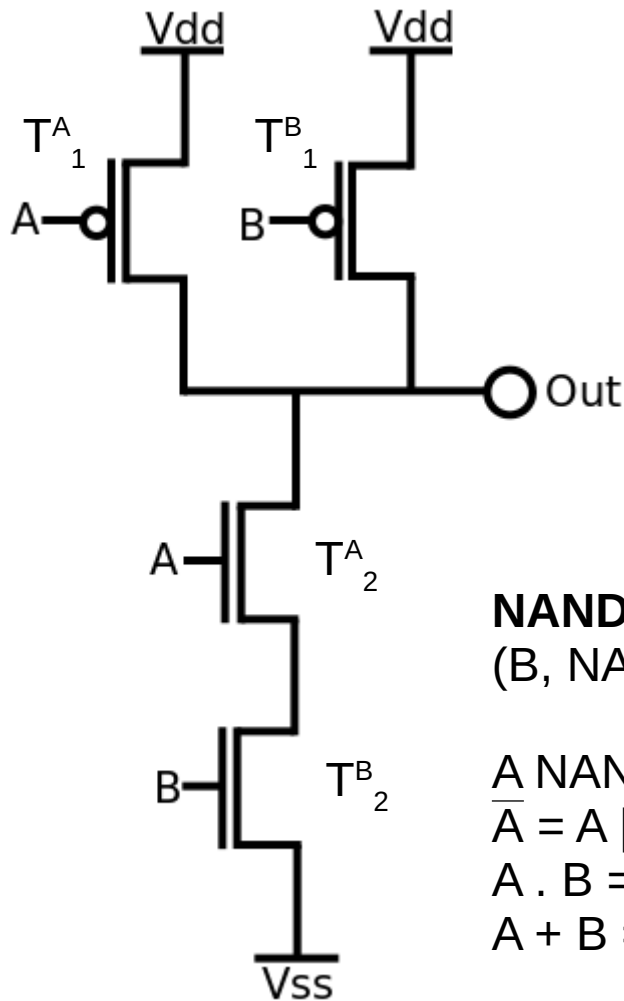

**NAND implementation**  
(B, NAND) complete group

$$A \text{ NAND } B = A | B = \overline{A \cdot B}$$

$$\overline{A} = A | A$$

$$A \cdot B = (A | A) | (B | B)$$

$$A + B = (A | B) | (A | B)$$

The same with NOR.

Vdd = 1

Vss = 0

when A = 1 and B = 1

$T_{11}^A, T_{11}^B$  off

$T_{22}^A, T_{22}^B$  on

Out = 0

when A = 0 and B = 1

$T_{11}^A, T_{22}^B$  on

$T_{11}^B, T_{22}^A$  off

Out = 1

when A = 1 and B = 0

$T_{11}^A, T_{22}^B$  off

$T_{11}^B, T_{22}^A$  on


Out = 1

when A = 0 and B = 0


$T_{11}^A, T_{11}^B$  on

$T_{22}^A, T_{22}^B$  off

Out = 1


 


# Composing gates to make a circuit

 


$$F_{\text{cout}}(A, B, C_{\text{in}}) = \overline{A}BC + A\overline{B}C + AB\overline{C} + ABC$$
  
$$F_S(A, B, C_{\text{in}}) = \overline{A}B\overline{C} + \overline{A}BC + A\overline{B}\overline{C} + ABC$$







 

 
# Designing a basic circuit

- identify inputs
- identify outputs → function to implement
- write a truth table for each function / output
- write the equation for each function  
(using conjunctive or disjunctive normal form)
- implement the circuit using AND / OR / NOT gates  
(automatic)
- build the circuit using transistors  
(synthesis – mostly automatic)


  
# Composing circuits to make bigger circuits



$$A = A_3 A_2 A_1 A_0$$

$$B = B_3 B_2 B_1 B_0$$


$$S = S_0 S_2 S_1 S_0$$

$$S_0 = A_0 + B_0 + C_{in}$$





$$S_1 = A_1 + B_1 + C_{out,0}$$


$$S_2 = A_2 + B_2 + C_{out,1}$$

$$S_3 = A_3 + B_3 + C_{out,2}$$



 


# Arithmetic circuits

    

 

# Useful circuit

   





 
# Overview

- Introduction
- Making basic circuits
- **Making the memory**
- Making the processor
- Conclusion







# 1-bit memory: flip-flop

  



| $S^t$ | $R^t$ | $Q^{t+1}$ | $\overline{Q}^{t+1}$ |
|-------|-------|-----------|----------------------|
| 1     | 1     | $Q^t$     | $\overline{Q}^t$     |
| 1     | 0     | 0         | 1                    |
| 0     | 1     | 1         | 0                    |
| 0     | 0     | X         | X                    |

 

 
$$A \text{ NAND } B = \overline{A \cdot B}$$




# D flip-flop

  

| $D^t$ | $Cp^t$ | $Q^{t+1}$ | $\overline{Q}^{t+1}$ |
|-------|--------|-----------|----------------------|
| X     | 1      | $Q^t$     | $\overline{Q}^t$     |
| 0     | 0      | 0         | 1                    |
| 1     | 0      | 1         | 0                    |

 


(chornogram)

 

# Von Neuman machine: control unit automaton

## loop

 
- (0) read instruction
- (1) read operands
- (2) compute
- (3) write result




| $Q_1^t$ | $Q_0^t$ | $Q_1^{t+1}$ | $Q_0^{t+1}$ | $D_1^t$ | $D_0^t$ |
|---------|---------|-------------|-------------|---------|---------|
| 0       | 0       | 0           | 1           | 0       | 1       |
| 0       | 1       | 1           | 0           | 1       | 0       |
| 1       | 0       | 1           | 1           | 1       | 1       |
| 1       | 1       | 0           | 0           | 0       | 0       |


$$D_0^t = \overline{Q_0^t}$$

 
$$D_1^t = \overline{Q_1^t} Q_0^t + Q_1^t \overline{Q_0^t}$$



 



# Von Neuman machine: control unit

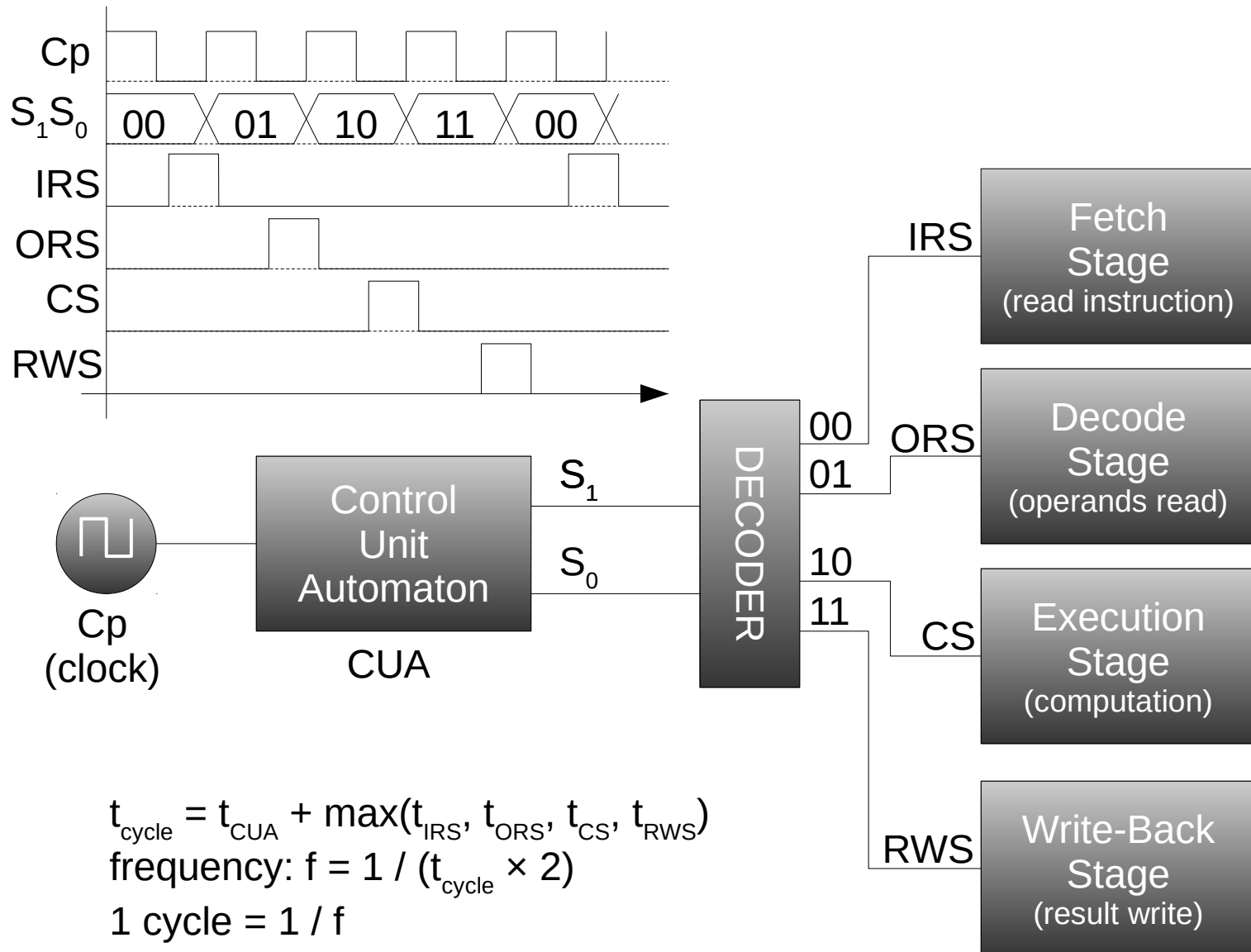

 

  
# Hardware register


- machine word =  $n$  bit
  - $n = 64$  in laptop
  - $n = 8 / 16 / 32 / 64$  in embedded systems
- hardware register
  - set of D flip-flop
  - storage for a word
  - $Cp$  = set signal
- read operation
- write operation
  - set value on  $D$
  - set 0 on  $\overline{W}$






 


# Register bank (write operation)

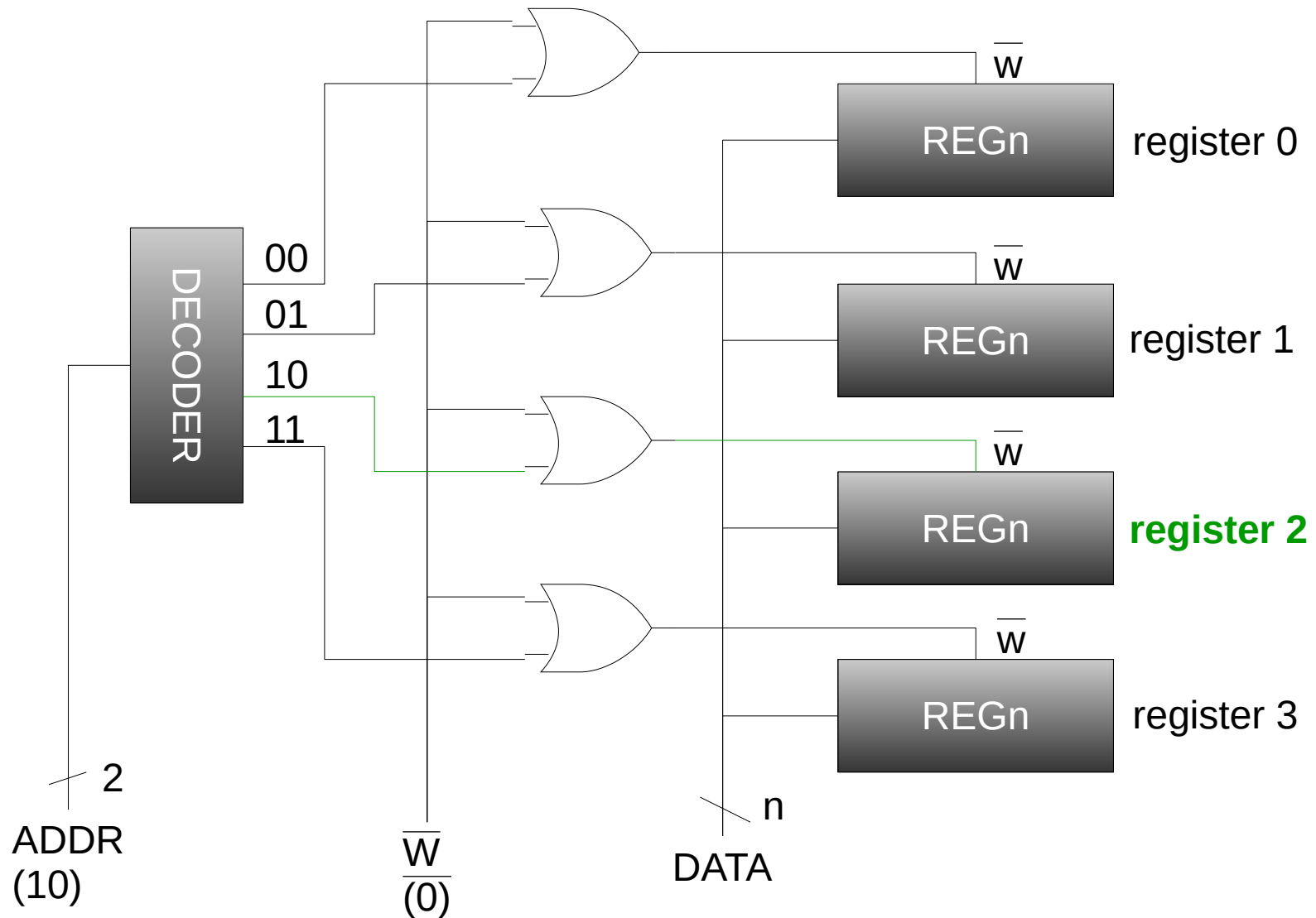

 


 
# Register bank (read operation)

- combination of register outputs?
  - wired OR – does not work (electronic properties)
  - n multiplexers (for n-bits)
  - tristate buffer – OK




| A | B | C            |
|---|---|--------------|
| X | 0 | Z (high imp) |
| 0 | 1 | 0            |
| 1 | 1 | 1            |

 

 

# System bus

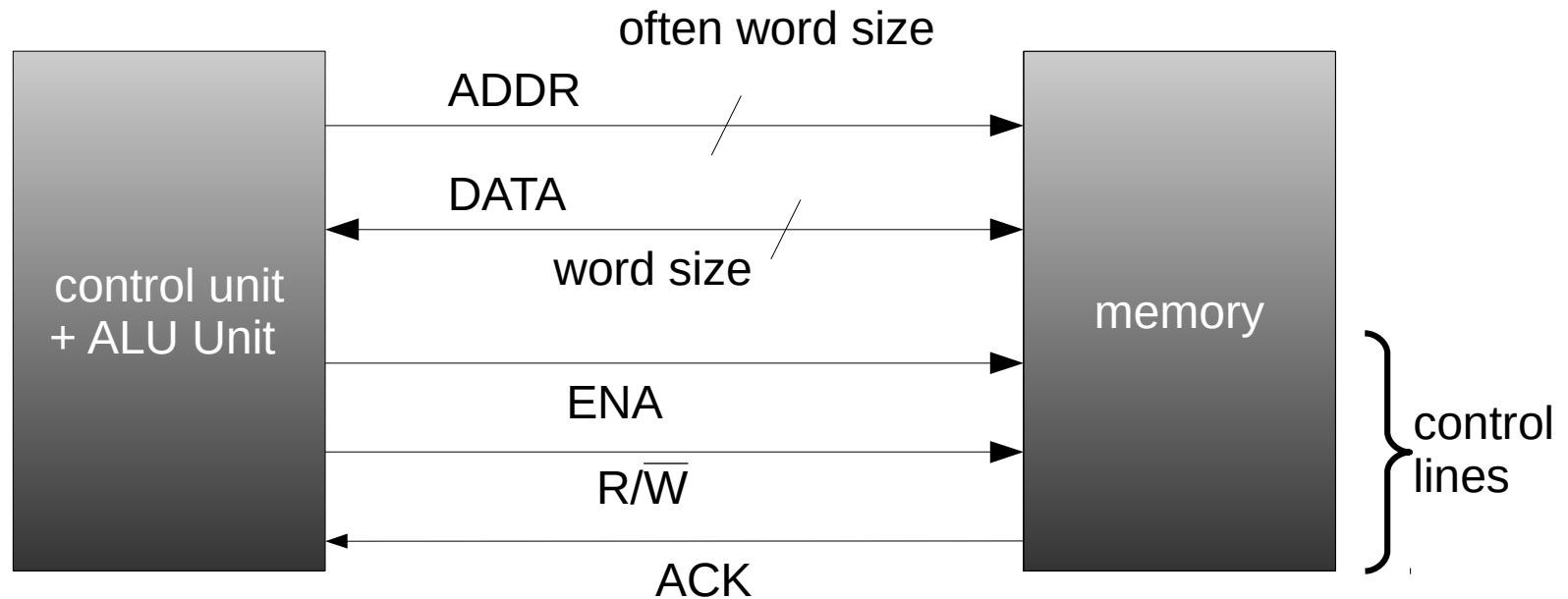


## **write word $w$ to address $a$**


- put  $w$  on DATA,  $a$  on ADDR and  $R/\overline{W}$  to 0
- then set ENA to 1
- wait for ACK set to 1 and reset ENA

 
## **read word $w$ to address $a$**

- put  $a$  on ADDR and  $R/\overline{W}$  to 1
- then set ENA to 1
- wait for ACK set to 1
- then reset ENA and read  $w$  from DATA



# Architecture of memory

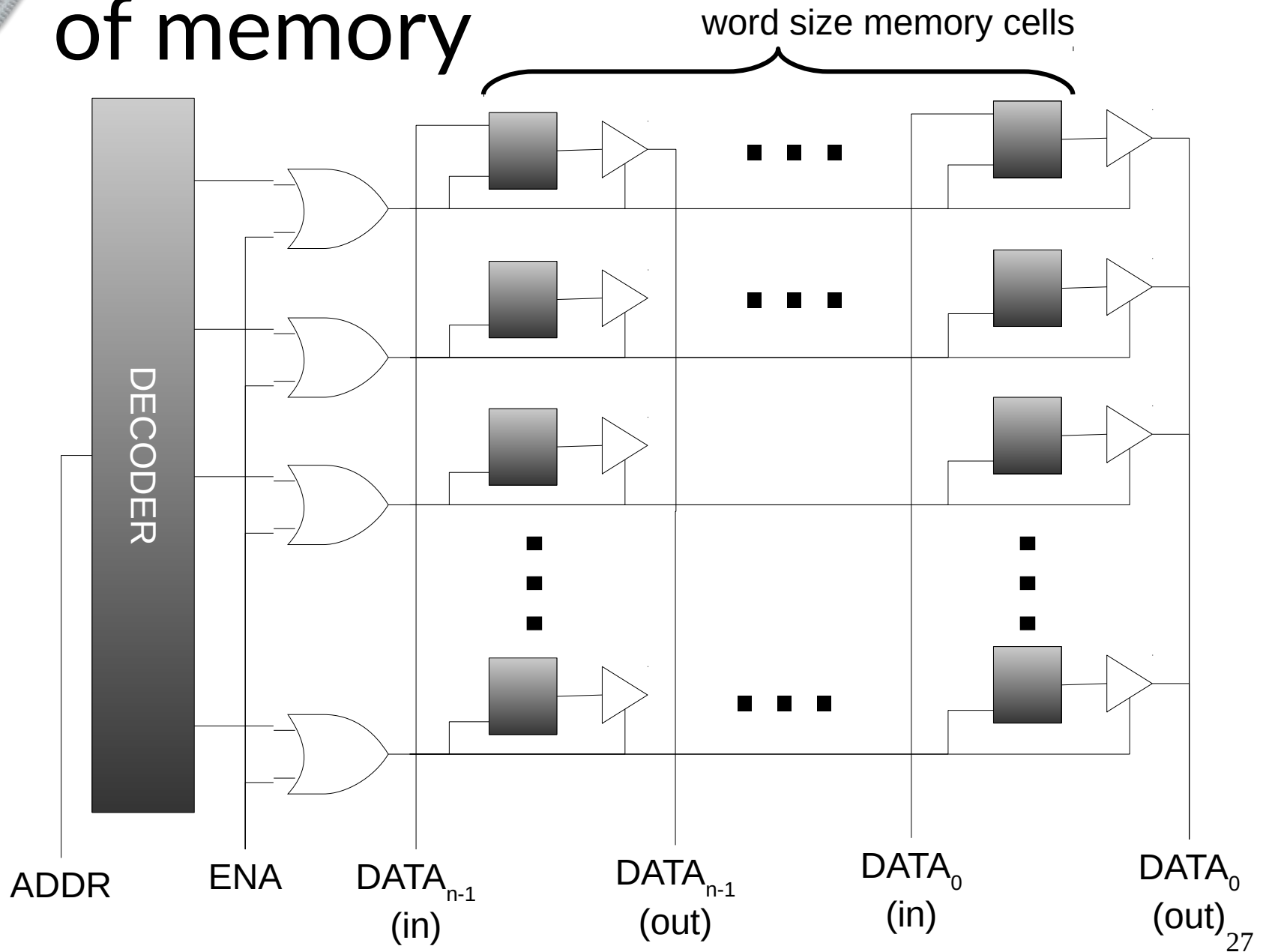


 
 
# Memory types


- memory cell = D flip-flop (volatile)
  - SRAM (Static Random Access Memory)
  - very fast but requires 8 transistor / cell
- memory cell = 1 transistor + 1 capacitor (volatile)
  - DRAM (Dynamic Random Access Memory)
  - slow and cheap (often called main memory)
  - different technology as microprocessor => different chip
- memory cell = 1 fuse (non-volatile)
  - PROM (Programmable Read-Only Memory)
  - burnt = 0, non-burnt = 1
- memory cell = flash memory cell (non-volatile)
  - EEPROM (Electrically Erasable Programmable ROM)
  - write very slow and by blocks
  - same technology as SSD or USB key





 
# DRAM memory cell

- capacitor
  - empty  $\rightarrow 0$
  - loaded  $\rightarrow 1$
- read
  - charge moved to a buffer (D flip-flop)
  - capacitor emptied
    - $\rightarrow$  need for reload
- write
  - capacitor is emptied
  - new value is stored
- refresh
  - capacitor charge is leaking  $\rightarrow$  loss of value
  - from time to time  $\rightarrow$  word is read and rewritten
  - operations suspended during this time



 


# Memory performances

- $t_{\text{access}}$  – time between start operation and end operation
- $t_{\text{cycle}}$  – time between 2 operations
- SRAM, PROM, flash
  - $t_{\text{access}} = t_{\text{cycle}}$
- DRAM
  - $t_{\text{cycle}} = t_{\text{access}} + t_{\text{rewrite}}$
  - $t_{\text{access}}^{\text{normal}} = t_{\text{access}}$  – most of the time
  - $t_{\text{access}}^{\text{refresh}} = t_{\text{access}} + t_{\text{refresh}}$  – during a refresh cycle
  - $t_{\text{refresh}}$  – depends on the refresh policy of the memory (one line, whole memory, several lines, etc)



 
# Overview


- Introduction
- Making basic circuits
- Making the memory
- **Making the processor**
- Conclusion




# Implementing the Von Neuman machine

 


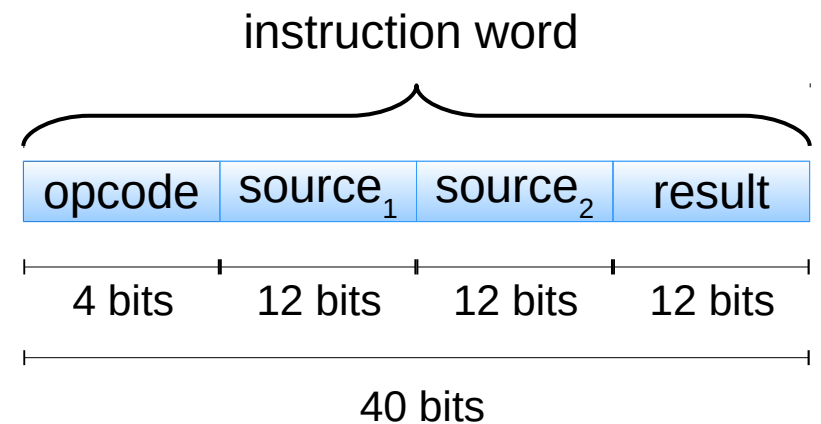
- instruction
  - operation (add, subtract, etc)
  - first operand address
  - second operand address
  - result address



 


# Arithmetic & Logic Part

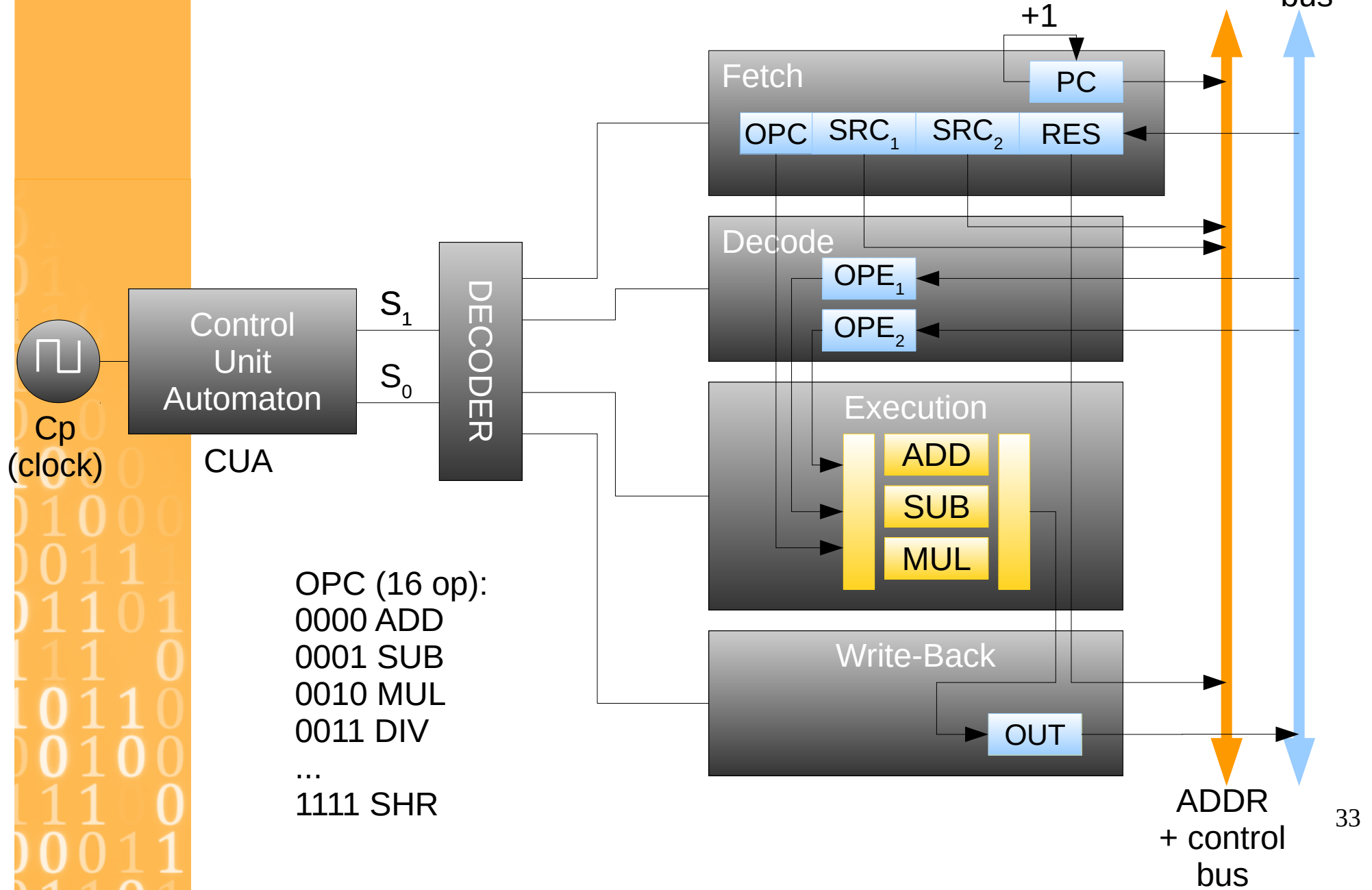

 


 
# Issues with Von Neuman machine

- memory is limited by operand address encoding
  - 12 bits → 4,096 addressable word
  - bigger memory → bigger instruction word
- machine is slow
  - bottleneck = access to memory
  - 4 accesses / instruction: instruction word + operand 1 + operand 2 + result
  - several cycles required
    - setting the address (+ data)
    - reading data + waiting acknowledge



# Register Bank

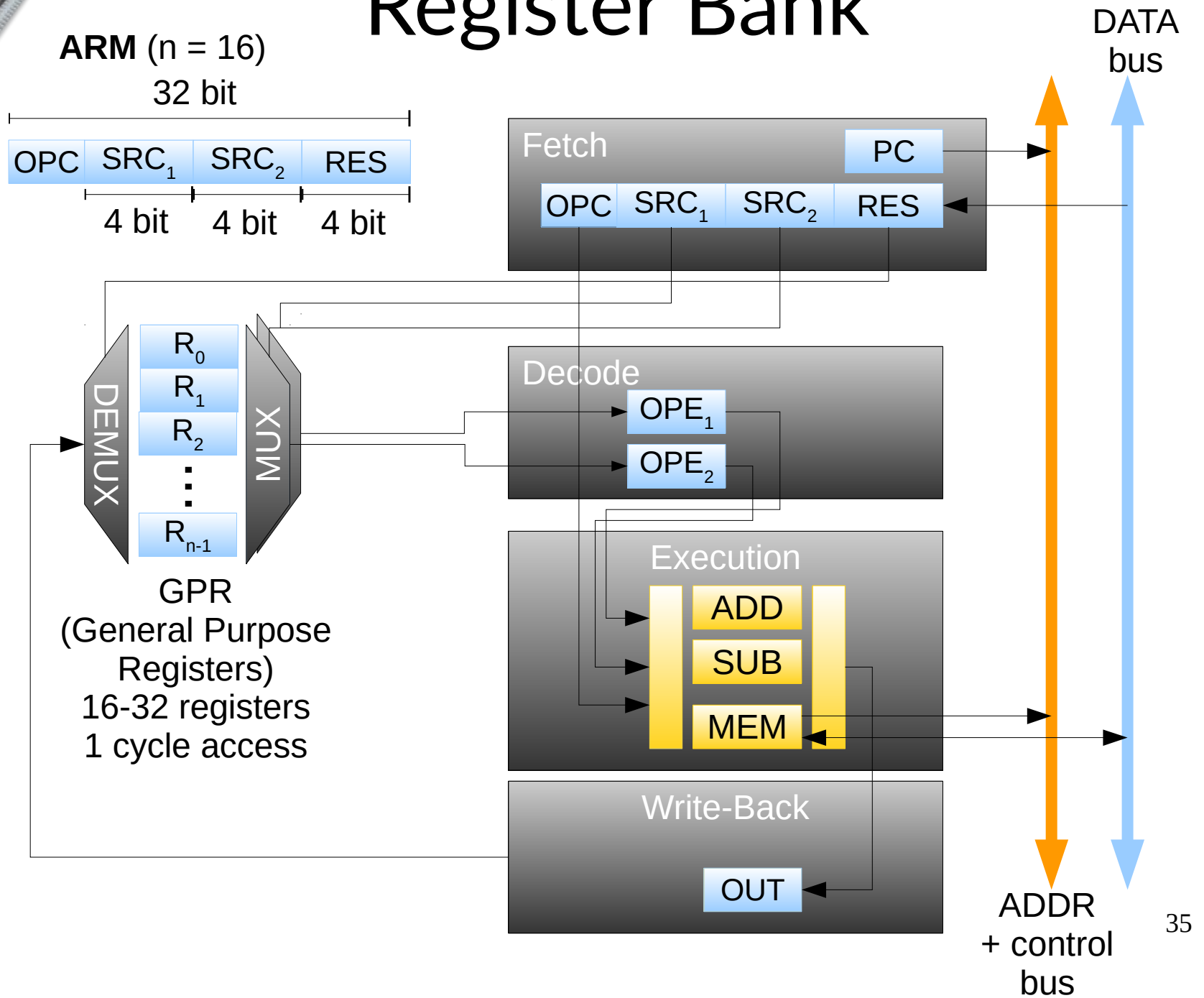

 

# Programming this machine (ARM example)


compute  $(R0 + R1 + R2 + R3)/4$

- ARM case
  - 1 instruction = 32-bit = 4 bytes
  - PC incremented of 4
- sequential behaviour
  - read instruction at PC
  - $PC \leftarrow PC + 4$
  - perform it in the execution unit
- program =
  - sequence of instructions
  - at address  $a$  in memory
  - execution =  $PC \leftarrow a$

|              |                |
|--------------|----------------|
| $a = 0x1000$ | ADD R4, R0, R1 |
| 0x1004       | ADD R4, R4, R2 |
| 0x1008       | ADD R4, R4, R3 |
| 0x100C       | MOV R5, #4     |
| 0x1010       | DIV R4, R4, R5 |

main memory



 

# Storing variables/array in memory


- select place to store the data
- build the address in GPR
- perform the memory access
- use the read data

```
int t[4];  
int s = t[0] + t[1] + t[2] + t[3];
```

```
MOV R0, #0           @ R0 ← 0 (= s)  
MOV R1, #0x2000      @ R1 ← 0x2000 (@t[0])  
LDR R2, [R1]  
ADD R0, R0, R2        @ R0 ← R0 + t[0]  
ADD R1, R1, #4        @ R1 ← R1 + 4 (@t[1])  
LDR R2, [R1]  
ADD R0, R0, R2        @ R0 ← R0 + t[0]  
ADD R1, R1, #4        @ R1 ← R1 + 4 (@t[2])  
...
```


memory


|        |      |
|--------|------|
| 0x2000 | t[0] |
| 0x2004 | t[1] |
| 0x2008 | t[2] |
| 0x200C | t[3] |

 
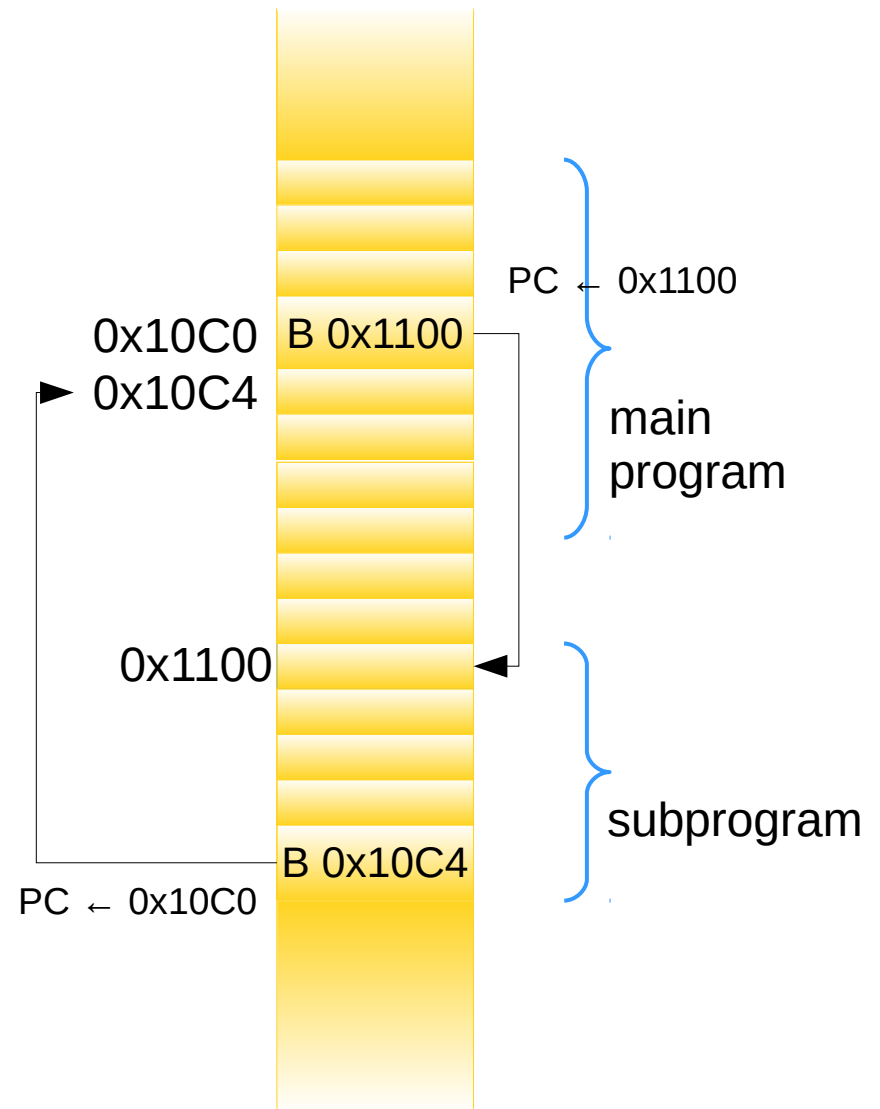
# Managing the control

- PC = address of instruction to execute
  - $PC \leftarrow PC + 4 =$  sequential execution
  - $PC \leftarrow a =$  select a different sequence to execute
- implementing a sub-program




 

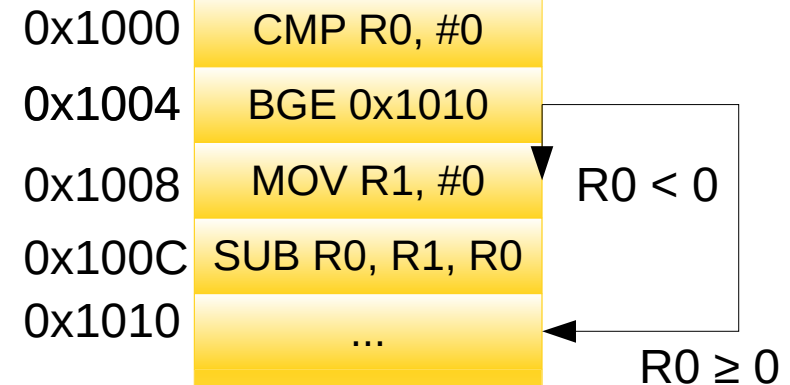
# Conditional execution

- while / if requires condition
- `CMP Ri, Rj`
  - compare R<sub>i</sub> and R<sub>j</sub>
  - store result in status register SR
- conditional branch
  - condition true → perform the branch
  - condition false → go on in sequence

```
int abs(int x) {  
    if(x < 0)  
        x = -x;  
    return x;  
}
```




GE = Greater or Equal

 
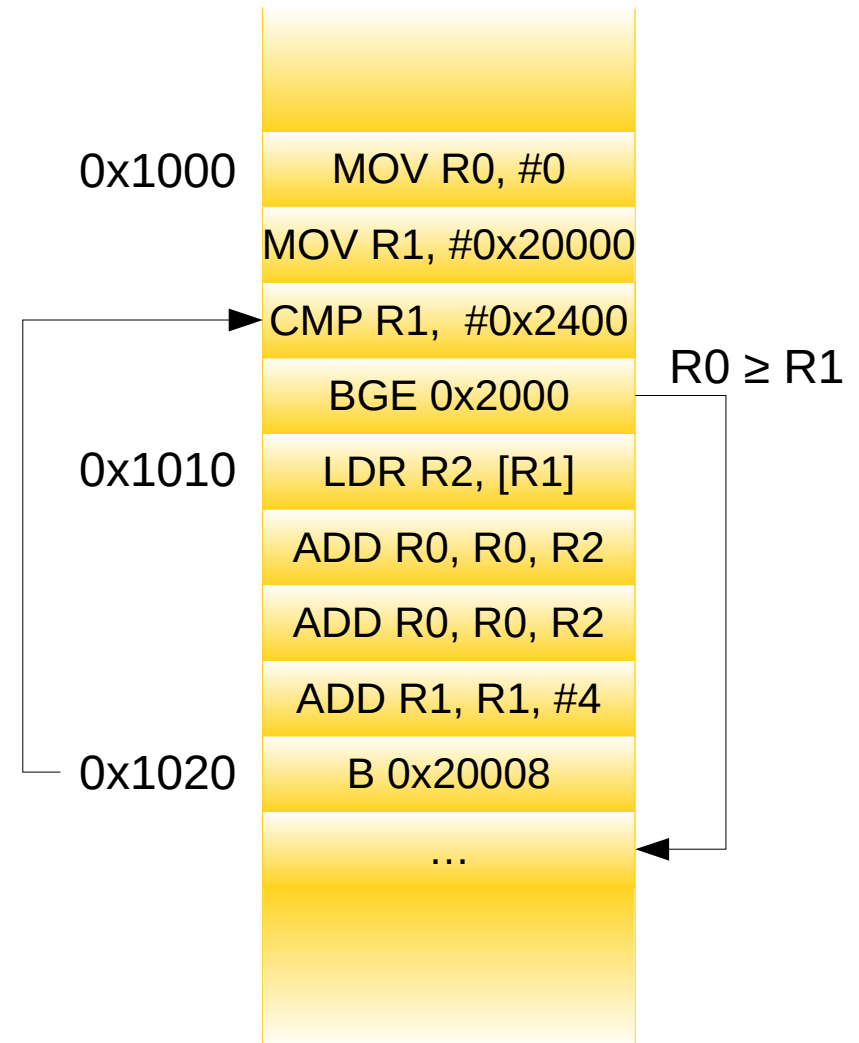
# Loop implementation

- looping =
  - restarting the same sequence of code = branch back
  - stopping = branching out when the condition is true


```
int t[256];  
s = 0;  
for(i = 0; i < 256; i++)  
    s = s + t[i];
```




 
# Overview

- Introduction
- Making basic circuits
- Making the memory
- Making the processor
- **Conclusion**



# Conclusion

- how to build a microprocessor
  - transistor → Boolean algebra → logic gates → binary function
  - binary function → basic operations (addition, etc)
  - logic gates → flip-flop → register → register bank → memories
  - control unit, Arithmetic & Logic Unit → microprocessor
- now
  - how to drive input / output (outside world)
  - how to improve the performances of the microprocessor
    - computation acceleration
    - memory footprint reduction